PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE-411043



Department of Computer Engineering

CLASS: S.E. COMP SUBJECT: DEL

EXPT. NO. : 9 DATE :

TITLE : PSEUDO RANDOM NUMBER GENERATOR CIRCUIT

OBJECTIVE:

1. Design and Implement the Pseudo Random number generator circuit using IC-74LS194 and verify its truth-table.(Use Left Shift)

2. Design and implement the Pseudo Random number generator circuit using IC-74LS76 and verify its truth-table(Use Right Shift)

APPARATUS

Digital-Board, GP-4 Patch-Cords, IC-74LS194, IC-74LS86

THEORY:

Register is a sequential logic device, which can be used to store the number of bits. Register whose internal bits can be shifted towards right and left is called as shift register. IC-74HC194 is a bi-directional universal shift register. This is called universal shift register because it performs all modes of operations of shift register.

IC-74HC194 provides four different modes of operation:

1) Serial in Serial Out. (SISO) 2) Serial in Parallel out (SIPO)


3) Parallel In Serial out (PISO) 4) Parallel in Parallel out (PIPO)

IC-74HC194 can be used to implement pulse train generator, ring counter, twisted ring counter, Random number generator circuit etc.



Department of Computer Engineering

PIN Diagram:

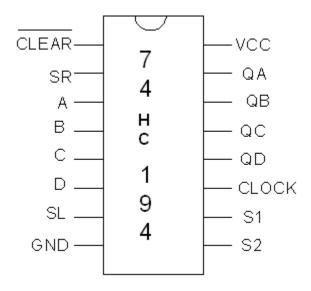

PROCEDURE :

- 1. Make the connections as per the Logic circuit of Pseudo Random number generator circuit using Left shift and Verify its Truth Table.
- 2. Make the connections as per the Logic circuit of Pseudo Random number generator circuit using Right shift and Verify its Truth Table.

Design of Pseudo Random Number Generator Circuit using Left Shift

Output				Decimal Equivalent	
QA	Qв	Qc	Q _D		

P:F-LTL UG/03/R1 9.2 DEL



PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE -411043

Department of Computer Engineering

	-:-	4:-	
LO	aic	ala	gram

P:F-LTL_UG/03/R1 9.3 DEL



PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE -411043

Department of Computer Engineering

Design of Pseudo Random Number Generator Circuit using Right Shift

Output				Decimal
QA	Qв	Qc	\mathbf{Q}_{D}	Equivalent

P:F-LTL_UG/03/R1 9.4 DEL



PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE-411043

Department of Computer Engineering

Logic Gates / MSI Device required for Implementation:

Sr.No.	Title	Name of the IC	Number of Gates required	IC Required
01	Pseudo Random Number generator circuit using Left and Right shift			



PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE -411043

Department of Computer Engineering

CONCLUSION:

REFFRENCE:

- 1. R.P.Jain "Modern Digital Electronics" TMH 4th Edition
- 2. D.Leach, Malvino, Saha, "Digital Principles and Applications", TMH

Subject teacher Sign with Date

Remark