



Department of Computer Engineering

CLASS: S.E.COMP

SUBJECT :DEL

EXPT. NO.:4

DATE:

TITLE : MULTIPLEXER / DEMULTIPLEXER

OBJECTIVE :

1. Verification of Function table of IC-74LS153
2. Design and Implement 8:1 MUX using IC-74LS153 and verify its truth Table
3. Realization of the following Boolean expression using IC-74153 and verify its truth-Table

$$F(A,B,C,D)=\sum m(\quad)$$

4. Verification of Function table of IC-74LS138
5. Realization of the following Boolean expression using IC-74138 and verify its truth-Table

$$F(A,B,C)=\sum m(\quad)$$

APPARATUS :

Digital-Board, GP-4Patch-Cords, IC-74LS32, IC-74LS08 / IC-74LS04 / IC-74LS153/IC-741LS38 and Required Logic gates if any.

THEORY :


Multiplexer is a combinational logic device, w h i c h has many input & one output, this output can be selected according to select input. IC-74LS153 is Dual 4:1 MUX. It is a 16-pin dual in-line packaged IC, which has two enable pins (STROBE Active Low). We can design 8:1 MUX using cascading of Two 4:1 MUX. This is achieved with the help of enable / strobe inputs and multiplexer tree is designed. To implement 8:1 MUX we need

Department of Computer Engineering

3 select lines and one output. Use dual 4:1 MUX for select lines 2 are common, use enable pin for 3rd select line. Connect the first strobe of first 4:1 MUX and the second strobe of second 4:1 MUX through one Inverter. This is 3rd select line only one 4:1 MUX will become active at one time. Connect outputs of 2 -MUX to OR gate so that we get one output .

De-Multiplexer/Decoder is a combinational logic device, which has one input & many output, one output can be selected according to select input. IC-74LS138 is 3 to 8 Line Decoder/Demultiplexer. It is a 16-pin dual packaged IC, which has three enable pins (2-STROBE Active Low and one Active High). IC-74LS138 produces complementary output. i.e. the output of 74LS138 is Active Low. We can design any combinational circuits using IC-74LS138. DEMUX/Decoder performs reverse operation to that of Multiplexer

PIN DIAGRAM:

 



Department of Computer Engineering

PROCEDURE :

1. Make the connections as per the Pin diagram of IC-74LS153 and Verify its Truth Table.
2. Make the connections as per the Logic circuit of 8:1 MUX and Verify its Truth Table
3. Make the connections as per Logic circuit of the given function and Verify its Truth Table
4. Make the connections as per the pin diagram of IC-74LS138 and Verify its Truth Table
5. Make the connections as per the Logic circuit of given function and Verify its Truth Table

Design of Multiplexer

Function Table: IC-74LS153

Chip Enable I/P		Select Input		OUTPUT	
1E	2E	S1(MSB)	S0(LSB)	MUX-I (1Y)	MUX-2 (2Y)
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		

Logical Expression:



Department of Computer Engineering

Logic Diagram:

Design of 8:1 MUX.using IC-74LS153

Design Table:

S2_(MSB)	S1	S0_(LSB)	OUTPUT (Y)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



Department of Computer Engineering

Logical Expression:

Logic Diagram:



Department of Computer Engineering

Design of Realization of Boolean expression using IC-74LS153

$$F(A,B,C,D)=\Sigma(\quad)$$


(LSB Variable Reduction Method)

Decimal Equ.	A _(MSB) (s2)	B (s1)	C (s0)	D _(LSB)	OUTPUT Y	Derived Logic
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		
8	1	0	0	0		
9	1	0	0	1		
10	1	0	1	0		
11	1	0	1	1		
12	1	1	0	0		
13	1	1	0	1		
14	1	1	1	0		
15	1	1	1	1		



Department of Computer Engineering

Logic Diagram:

 



Department of Computer Engineering

Design of Realization of Boolean expression using IC-74LS153

$$F(A,B,C,D)=\Sigma(\quad)$$

(MSB Variable Reduction Method)

Decimal Equ.	A ^(MSB) (s2)	B (s1)	C (s0)	D ^(LSB)	OUTPUT Y	Derived Logic
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		
8	1	0	0	0		
9	1	0	0	1		
10	1	0	1	0		
11	1	0	1	1		
12	1	1	0	0		
13	1	1	0	1		
14	1	1	1	0		
15	1	1	1	1		



Department of Computer Engineering

Implementation Table:

--

Logic Diagram:

--



Department of Computer Engineering

Design of Decoder

Function Table : IC-74LS138

<i>Chip Enable Input</i>			<i>Active Low Output</i>							
G₃	G₂	G₁	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
1	0	0								
1	0	0								
1	0	0								
1	0	0								
1	0	0								
1	0	0								
1	0	0								
1	0	0								

Logical Expression:



Department of Computer Engineering

Logic Diagram:

Design of Realization of Boolean expression using IC-74LS138

$$F(A,B,C,D)=\Sigma(\quad)$$

Decimal Equ.	A	B	C	OUTPUT F(A,B,C)
0	0	0	0	
1	0	0	1	
2	0	1	0	
3	0	1	1	
4	1	0	0	
5	1	0	1	
6	1	1	0	
7	1	1	1	

Logical Expression:



Department of Computer Engineering

Logic Diagram:

--

Logic Gates / MSI Device required for Implementation:

Sr.No.	Title	Name of the IC	Number of Gates required	IC Required
01	Design of 8:1 MUX.			
02	Realization of Boolean expression using LSB reduction method			



Department of Computer Engineering

03	Realization of Boolean expression using MSB reduction method			
04	Realization of Boolean expression using Decoder IC			

CONCLUSION:

REFERENCE:

1. R.P.Jain "Modern Digital Electronics" TMH 4th Edition
2. D.Leach,Malvino,Saha,"Digital Principles and Applications",TMH

Subject teacher Sign with Date

Remark